

Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA
(An Autonomous Institute)

Affiliated to Dr. A.P. J. Abdul Kalam Technical University, Uttar Pradesh, Lucknow

Course: B.Tech

Branch: CSE/CS/IT/M.Tech Integrated/Regional

Semester: IIIrd

Sessional Examination: First

Subject Name: Digital Logic and Circuit Design Year- (2022-2023)

Time: 1.15 Hours

Max. Marks: 30

General Instructions:

- This Question paper consists ofpages &questions. It comprises three Sections -A, B, & C. You are expected to answer them as directed.
- Section A-Q.No- 1 is of one 1 mark each & Q.No- 2 carries 2 mark each.
- Section B-Q. No- 3 carries 5 marks each.
- Section C-Q.No-4 & 5 carries 6 marks each. Attempt any one part a or b

SECTION – A			[08 Marks]	
1. All questions are compulsory-			(4×1=4)	
a.	Binary equivalent of gray code 101011 is:		(1)	CO-1
	a. 110010			
	b. 101010			
	c. 110110			
	<input checked="" type="checkbox"/> d. 110011			
b.	The value of (011010101.110) ₂ in octal and hexadecimal are:		(1)	CO-1
	a. (236.6) ₈ and (D5.B) ₁₆			
	b. (235.6) ₈ and (D5.C) ₁₆			
	<input checked="" type="checkbox"/> c. (325.6) ₈ and (D5.C) ₁₆			
	d. (225.6) ₈ and (D5.C) ₁₆			
c.	Excess-3 code of 739 is:		(1)	CO-1
	<input checked="" type="checkbox"/> a. 1010 0110 1100			
	b. 1101 1001 1000			
	c. 1101 0110 1100			
	d. 1010 1001 1000			
d.	Determine the value of base x if $(50)_x = (203)_4$		(1)	CO-

		a. 6 b. 5 c. 7 d. 8		1
2.	All questions are compulsory-			
	a.	$(347)_{10} = ()_2 = ()_8 = ()_{16} = ()_{BCD}$	(2×2=4)	
			(2)	CO-1
	b.	Given the two binary numbers $X = 1010101$ and $Y = 1001011$, perform the subtraction $X-Y$ using 1's complements.	(2)	CO-1
SECTION – B				
3.	Answer any <u>two</u> of the following-		[10Marks]	
	a.	Add in BCD 6710 and 431810.	(2×5=10)	
			(5)	CO-1
	b.	Simplify the expression using DEMORGAN'S THEOREM: $[a(b+c)+a'b]$	(5)	CO-1
	c.	Receiver receives the hamming code 1111001, check whether the data received is correct if not, check the error and correct it.	(5)	CO-1
SECTION – C				
4	Answer any <u>one</u> of the following-		[12Marks]	
	a.	What is cyclic Code? Prove that (110, 101, 011) is a cyclic code.	(1×6=6)	
			(6)	CO-1
	b.	Minimise the following function in POS minimal form using K-Maps: $F(A, B, C, D) = M(6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$	(6)	CO-1
5.	Answer any <u>one</u> of the following-		(1×6=6)	
	a.	Simplify the following Boolean functions using the Karnaugh map: $F(w,x,y,z) = \sum m(0,1,2,4,5,12,13,14) + \text{don't care conditions } \sum d(6,8,9)$	(6)	CO-1
	b.	The solution to the quadratic equation $k^2 - 11k + 22 = 0$ is $k = 3$ and $k = 6$. What is the base of number systems?	(6)	CO-1

a. Explain Applications of Multiplexer.

(2) CO2

b. Define combinational logic.

(2) CO2

SECTION – B

3. Answer any two of the following-

[10Marks]

(2×5=10)

a. Draw the truth table and circuit diagram of the 8 to 3 encoder. (5) CO2

b. Implement 3:8 decoder using 2:4 decoders. (5) CO2

c. Draw the logic diagram of full subtractor and explain its operation. (5) CO2

SECTION – C

4 Answer any one of the following-

[12Marks]

(1×6=6)

a. Implement the following Boolean function using 8:1 multiplexer (6) CO2

$$F(A, B, C, D) = \sum m(0, 1, 2, 5, 7, 8, 9, 14, 15).$$

b. Draw a BCD adder and explain its working. (6) CO2

5. Answer any one of the following-

(1×6=6)

a. Explain about 2-bit Magnitude Comparator. (6) CO2

b. Design the combinational circuit of 4 Bit Parallel Adder? (6) CO2