
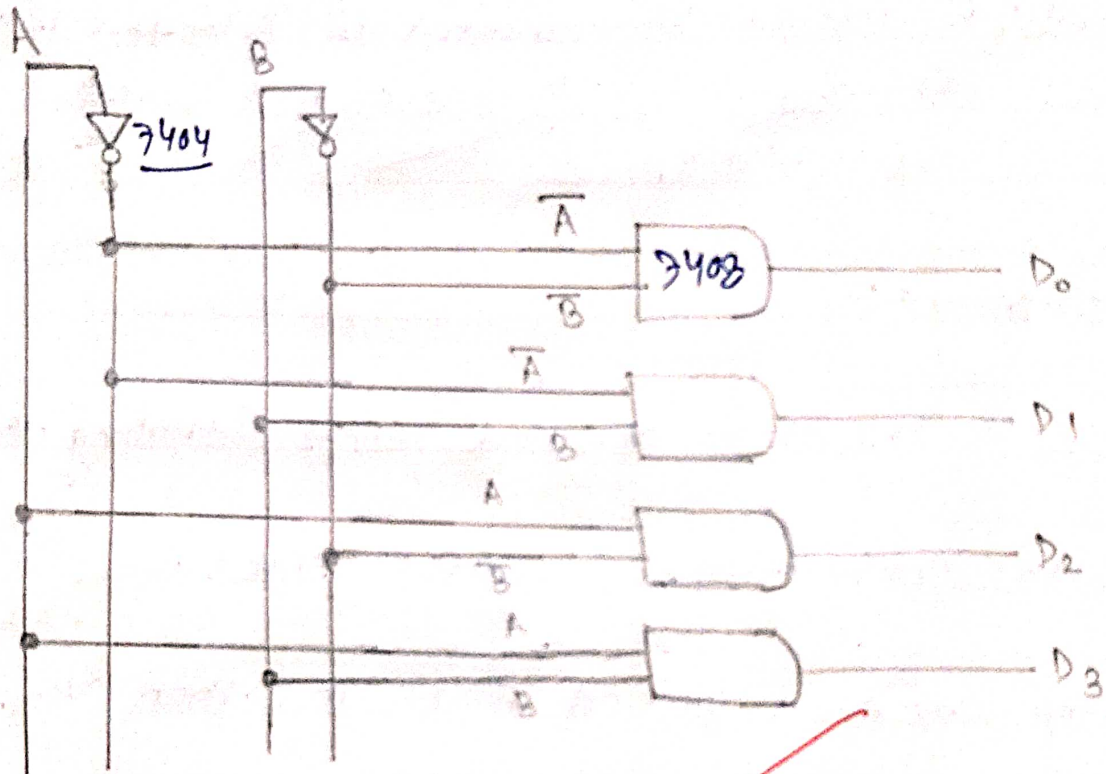


Logic Diagram.

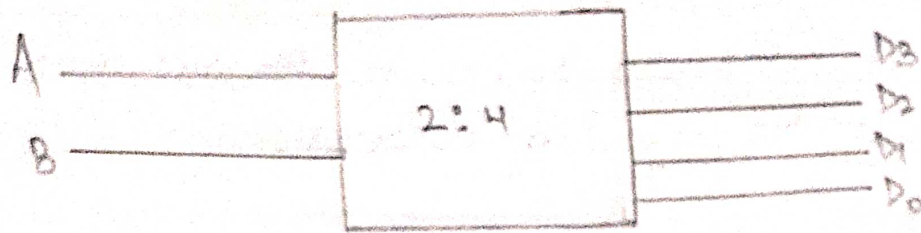

TT

EXPERIMENT NO. \rightarrow 5

Aim: Implementation of 2:4 encoder Using logic gates and Verify its truth table.

Apparatus Required:

S.No	Name of Component	Specification	Qty
1.	NOT Gate	7404	1
2.	AND Gate	7408	1
3.	LED	—	4
4.	Wires	—	As required
5.	Bread board	—	1
6.	Power Supply	5VDC	1

Theory:-

A decoder is a device which performs the operation as reverse of that of an encoder.

It is a Combinational Circuit that converts binary information from n input lines to a max^m of 2^n output lines.

In digital electronics, decoder can take the form of a multiple input - multiple output where the input and output codes are different.

Teacher's Signature : _____

Truth Table


INPUT		OUTPUT			
A	B	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1
		$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	AB

In case of decoding all combination of two bit decoding are required.

Result: 2:4 decoder has been implemented and the truth table is verified.

Precautions:-

- i) Check all the ICs before performing the experiment.
- ii) Connect ground first and then Vcc.
- iii) Switch off the power supply before making the connection.
- iv) All the connections should be tight.

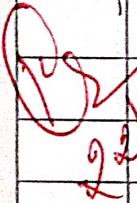 22/11/2021